

1 Simple quadrature decoder. Gary Dickinson 2/14/2020

This is a very simplified version of Lorne Van Dusen's code.  
I just got rid of the stuff that didn't add value.

This version uses ladder logic COUNTERS. I agree with Lorne's observation that the ladder logic COUNTERS are a bit obtuse. A single COUNTER can work with values between 0 and 9999. It is possible to extend the count range by cascading COUNTERS. I used 2 counters to get a count range 0 to 99,999,999.

2 1st.Scan LoadCnts 2 {dCusF}

3 Reset r3 ZeroCnts 1 {dCusF}

4 The following two rungs detect the direction based on the state of the A input at the rising edge of the B input. CntUP or CntDN will be active for one scan time.

5 B r2 A r1 CntUP r4 (RLY)

6 B r2 A /r1 CntDN r5 (RLY)

7 The following 2 rungs increment a cascaded pair of "up" COUNTERS. Each PLC COUNTER can count from 0..9999. When the first counter overflows from 9999 to 0 the 2nd COUNTER is incremented.

8 CntUP r4 Digits3\_0 c9 [Upctr]

9 CntUP r4 Digits3\_0 c9 Digits7\_4 c10 [Upctr]

10 The following 2 rungs increment a cascaded pair of "down" COUNTERS.

11 CntDN r5 Digits3\_0 c9 [DNctr]

